


## Verilog Lab Midterm Exam

### 1. NAND gate using 2:1 Multiplexers

Truth Table

A	B	NAND output
0	0	1
0	1	1
1	0	1
1	1	0

$$Y_{NAND} = \overline{A \cdot B} = 1$$

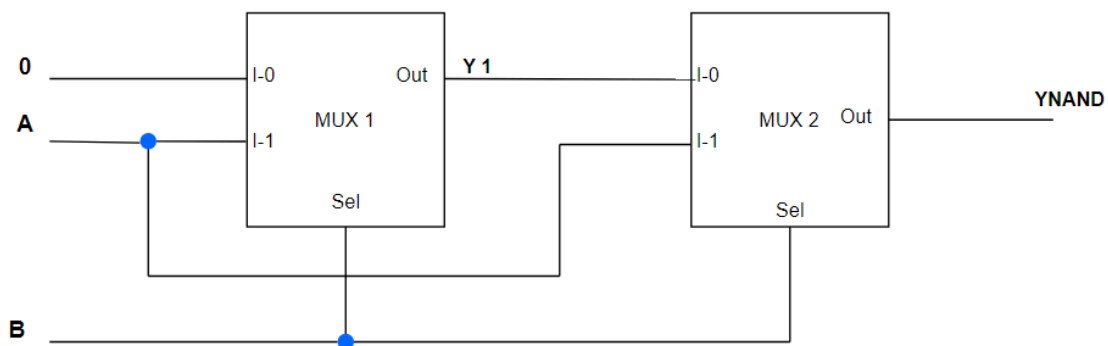

**NAND Gate using two Multiplexers**

### 2. RTL module

```
module swap_no_temp(
    input [7:0] A_in,
    input [7:0] B_in,
    input clk,
```

```

input reset,
output reg [7:0] A_out,
output reg [7:0] B_out
);

always @(posedge clk or posedge reset) begin
    if (reset) begin
        A_out = A_in; // Initialize A_out with A_in
        B_out = B_in; // Initialize B_out with B_in
    end else begin
        // Correct XOR Swap operation using blocking assignments
        A_out = A_out ^ B_out;
        B_out = A_out ^ B_out;
        A_out = A_out ^ B_out;
    end
end
endmodule

```

### **Testbench**

```

module tb_swap_no_temp;
    reg [7:0] A_in, B_in;
    reg clk, reset;
    wire [7:0] A_out, B_out;

    // Instantiate the swap module
    swap_no_temp uut (
        .A_in(A_in),
        .B_in(B_in),
        .clk(clk),
        .reset(reset), // Connect reset signal
        .A_out(A_out),
        .B_out(B_out)
    );

    // Clock generation
    always #5 clk = ~clk; // Clock toggles every 5 time units

    initial begin
        // Initialize inputs
        A_in = 8'hAA;

```

```

    B_in = 8'h55;
    clk = 0;
    reset = 1;    // Assert reset at the start

    // Release reset after some time
    #10 reset = 0;

    // Print the results
    $monitor("Time: %0t | A_in: %h | B_in: %h | A_out: %h | B_out: %h", $time, A_in,
    B_in, A_out, B_out);

    // Stop the simulation after some time
    #60;
    $finish;
end

endmodule

```

## Results

```

[2024-10-24 21:15:13 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
Time: 10 | A_in: aa | B_in: 55 | A_out: aa | B_out: 55
Time: 15 | A_in: aa | B_in: 55 | A_out: 55 | B_out: aa
Time: 25 | A_in: aa | B_in: 55 | A_out: aa | B_out: 55
Time: 35 | A_in: aa | B_in: 55 | A_out: 55 | B_out: aa
Time: 45 | A_in: aa | B_in: 55 | A_out: aa | B_out: 55
Time: 55 | A_in: aa | B_in: 55 | A_out: 55 | B_out: aa
Time: 65 | A_in: aa | B_in: 55 | A_out: aa | B_out: 55
testbench.sv:34: $finish called at 70 (1s)
Done

```

### 3. RTL module(TFF)

```

`timescale 1ns/1ps // Time unit is 1 nanosecond, precision is 1 picosecond

```

```

module T_FF (
    input wire T,    // Toggle input
    input wire RST,  // Reset input
    input wire CLK,  // Clock input
    output reg Q     // Output
);
    // Always block for T Flip-Flop behavior
    always @(posedge CLK or posedge RST) begin
        if (RST) begin

```

```

        Q <= 0;    // Reset output to 0
    end else if (T) begin
        Q <= ~Q;   // Toggle output
    end
end
endmodule

```

## Testbench

```
`timescale 1ns/1ps
```

```

module testbench;
    reg T;    // T input for the T Flip-Flop
    reg RST;  // Reset signal
    wire Q;   // Output of the T Flip-Flop

    // Instantiate the T Flip-Flop module
    T_FF tff (
        .T(T),
        .RST(RST),
        .Q(Q)
    );

    // VCD Dump to generate waveform
    initial begin
        $dumpfile("T_FF_waveform.vcd"); // Specify the VCD file name
        $dumpvars(0, testbench);        // Dump all variables in the testbench
    end

    initial begin
        // Initialize signals
        T = 0;
        RST = 1;

        // Apply reset
        #10 RST = 0; // Release reset
        #10 T = 1;   // Set T to 1
        #20 T = 0;   // Set T to 0
        #10 T = 1;   // Set T to 1 again
        #30 T = 0;   // Set T to 0
        #10 RST = 1; // Assert reset
    end
endmodule

```

```

    #20 RST = 0; // Release reset
    #10 T = 1; // Set T to 1 again
    #20 $finish; // End the simulation
end

// Display output
initial begin
    $monitor("Time: %0t | T: %b | RST: %b | Q: %b", $time, T, RST, Q);
end
endmodule

```

## Results

Log

Share

[2024-10-24 21:27:32 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&

unbuffer vvp a.out

```

Time:              0 | T: 0 | RST: 1 | Q: 0
Time:            10000 | T: 0 | RST: 0 | Q: 0
Time:            20000 | T: 1 | RST: 0 | Q: 0
Time:            25000 | T: 1 | RST: 0 | Q: 1
Time:            35000 | T: 1 | RST: 0 | Q: 0
Time:            45000 | T: 1 | RST: 0 | Q: 1
Time:            55000 | T: 1 | RST: 0 | Q: 0
Time:            60000 | T: 0 | RST: 0 | Q: 0
Time:            90000 | T: 1 | RST: 0 | Q: 0
Time:            95000 | T: 1 | RST: 0 | Q: 1
Time:           105000 | T: 1 | RST: 0 | Q: 0
Time:           115000 | T: 1 | RST: 0 | Q: 1
Time:           120000 | T: 0 | RST: 0 | Q: 1

```


Final Output: Q = 1

testbench.sv:44: \$finish called at 150000 (1ps)

Done

From: 0ps To: 140,000ps

Get Signals Radix Q Q 100% ◀ ▶ ◀ ▶ ▲ ▼ ✕

 

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

#### 4. Comparator module(Gate level)

```
module comparator_1bit (  
    input A,  
    input B,  
    output A_gt, // A > B  
    output A_eq, // A = B  
    output A_lt  // A < B  
);  
    wire not_A, not_B; // Intermediate wires for NOT operations  
  
    // Invert A and B  
    not(not_A, A);  
    not(not_B, B);  
  
    // A = B condition  
    wire eq1, eq2; // Intermediate signals for equality  
    and(eq1, not_A, not_B); // A and B both 0  
    and(eq2, A, B);        // A and B both 1  
    or(A_eq, eq1, eq2);    // A is equal to B  
  
    // A > B condition  
    and(A_gt, A, not_B);   // A is 1 and B is 0  
  
    // A < B condition  
    and(A_lt, not_A, B);   // A is 0 and B is 1  
endmodule
```

#### Testbench

```
module testbench;  
    reg A, B;          // Test inputs  
    wire A_gt, A_eq, A_lt; // Outputs from the comparator  
  
    // Instantiate the comparator  
    comparator_1bit comp (  
        .A(A),  
        .B(B),  
        .A_gt(A_gt),  
        .A_eq(A_eq),  
        .A_lt(A_lt)
```

```

);

initial begin
    // Test cases
    $monitor("A=%b, B=%b | A_gt=%b, A_eq=%b, A_lt=%b", A, B, A_gt, A_eq,
A_lt);

    // Test case: A = 0, B = 0
    A = 0; B = 0; #10;
    // Test case: A = 0, B = 1
    A = 0; B = 1; #10;
    // Test case: A = 1, B = 0
    A = 1; B = 0; #10;
    // Test case: A = 1, B = 1
    A = 1; B = 1; #10;

    // Finish simulation
    $finish;
end
endmodule

```

## Results

```

[2024-10-24 21:32:55 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
A=0, B=0 | A_gt=0, A_eq=1, A_lt=0
A=0, B=1 | A_gt=0, A_eq=0, A_lt=1
A=1, B=0 | A_gt=1, A_eq=0, A_lt=0
A=1, B=1 | A_gt=0, A_eq=1, A_lt=0
testbench.sv:28: $finish called at 40 (1s)
Done

```

## 5. Design Module DFF (Gate level)

```

module DFF_gate_level(
    output Q,
    output Q_bar,
    input D,
    input CLK
);
    wire D_bar;
    wire w1, w2, w3, w4;

    // Invert D

```

```

not (D_bar, D);

// NAND gates for the D flip-flop
nand (w1, D, CLK);    // First NAND gate
nand (w2, D_bar, CLK); // Second NAND gate
nand (w3, w1, w4);    // Third NAND gate (feedback)
nand (w4, w2, w3);    // Fourth NAND gate (feedback)

assign Q = w3;        // Output Q
assign Q_bar = w4;    // Output Q_bar (inverse of Q)

endmodule

Testbench
module testbench();
    reg D;            // Input for the D flip-flop
    reg CLK;          // Clock signal
    wire Q;           // Output Q
    wire Q_bar;       // Output Q_bar

    // Instantiate the D flip-flop
    DFF_gate_level dff (.Q(Q), .Q_bar(Q_bar), .D(D), .CLK(CLK));

    initial begin
        // Initialize signals
        CLK = 0;
        D = 0;

        // Open a VCD file for waveform dumping
        $dumpfile("waveform.vcd"); // Name of the VCD file
        $dumpvars(0, testbench);   // Dump all variables in this module

        // Monitor changes
        $monitor("Time: %0d | D: %b | CLK: %b | Q: %b | Q_bar: %b", $time, D, CLK, Q,
        Q_bar);

        // Test sequence
        #5 CLK = 1; D = 0; // Rising edge, Q should remain 0
        #5 CLK = 0;        // Falling edge
        #5 CLK = 1; D = 1; // Rising edge, Q should now be 1
    end

```



```

#5 CLK = 0;    // Falling edge
#5 CLK = 1; D = 0; // Rising edge, Q should now be 0
#5 CLK = 0;    // Falling edge
#5 CLK = 1; D = 1; // Rising edge, Q should now be 1
#5 CLK = 0;    // Falling edge
#5 CLK = 1; D = 0; // Rising edge, Q should now be 0
#5 CLK = 0;    // Final falling edge

#5 $finish;    // End the simulation
end

// Generate clock signal
always #5 CLK = ~CLK; // Toggle CLK every 5 time units
endmodule

```

## Results

```

[2024-10-24 20:50:50 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out


```

```

Time: 0 | D: 0 | CLK: 0 | Q: x | Q_bar: x
Time: 5 | D: 0 | CLK: 1 | Q: 0 | Q_bar: 1
Time: 10 | D: 0 | CLK: 0 | Q: 0 | Q_bar: 1
Time: 15 | D: 1 | CLK: 1 | Q: 1 | Q_bar: 0
Time: 20 | D: 1 | CLK: 0 | Q: 1 | Q_bar: 0
Time: 25 | D: 0 | CLK: 1 | Q: 0 | Q_bar: 1
Time: 30 | D: 0 | CLK: 0 | Q: 0 | Q_bar: 1
Time: 35 | D: 1 | CLK: 1 | Q: 1 | Q_bar: 0
Time: 40 | D: 1 | CLK: 0 | Q: 1 | Q_bar: 0
Time: 45 | D: 0 | CLK: 1 | Q: 0 | Q_bar: 1
Time: 50 | D: 0 | CLK: 0 | Q: 0 | Q_bar: 1
testbench.sv:30: $finish called at 55 (1s)

```

Done

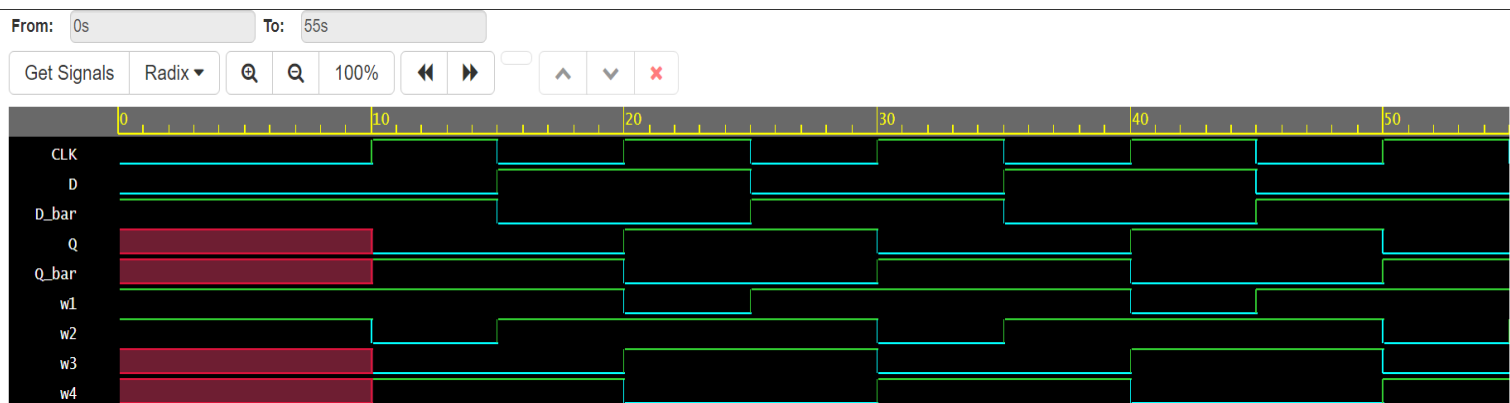

## 6. Design module

```
// UDP for AND gate
primitive and_udp (out, in1, in2);
    output out;
    input in1, in2;
```

```
    table
        // in1 in2 : out
        0  0  : 0;
        0  1  : 0;
        1  0  : 0;
        1  1  : 1;
    endtable
endprimitive
```

```
// UDP for OR gate
primitive or_udp (out, in1, in2);
    output out;
    input in1, in2;
```

```
    table
        // in1 in2 : out
        0  0  : 0;
        0  1  : 1;
        1  0  : 1;
        1  1  : 1;
    endtable
endprimitive
```

```
`timescale 1ns/1ps
```

```
module top_module (
    input A, B, C,
    output X, Y
);
```

```
    wire and1_out, and2_out; // Wires to connect intermediate signals
```

```
    // Instantiate AND gates
    and_udp U1 (and1_out, A, B); // First AND gate
    and_udp U2 (and2_out, A, C); // Second AND gate
```

```

// Instantiate OR gates
or_udp U3 (X, and1_out, and2_out); // First OR gate for output X
or_udp U4 (Y, B, C);              // Second OR gate for output Y

endmodule

```

### **Testbench module**

```

`timescale 1ns/1ps

```

```

module tb_top_module;

```

```

// Inputs

```

```

reg A;

```

```

reg B;

```

```

reg C;

```

```

// Outputs

```

```

wire X;

```

```

wire Y;

```

```

// Instantiate the top module

```

```

top_module uut (

```

```

    .A(A),

```

```

    .B(B),

```

```

    .C(C),

```

```

    .X(X),

```

```

    .Y(Y)

```

```

);

```

```

// Test stimulus

```

```

initial begin

```

```

    // Initialize inputs

```

```

    A = 0; B = 0; C = 0;

```

```

    #10;

```

```

    // Apply test cases

```

```

    A = 0; B = 0; C = 1;

```

```

    #10;

```

```

    A = 0; B = 1; C = 0;
    #10;

    A = 0; B = 1; C = 1;
    #10;

    A = 1; B = 0; C = 0;
    #10;

    A = 1; B = 0; C = 1;
    #10;

    A = 1; B = 1; C = 0;
    #10;

    A = 1; B = 1; C = 1;
    #10;

    // Finish simulation
    $finish;
end

// Monitor values for debugging
initial begin
    $monitor("Time = %0t | A = %b, B = %b, C = %b -> X = %b, Y = %b",
        $time, A, B, C, X, Y);
end

// Dump waveform data
initial begin
    $dumpfile("waveform.vcd"); // This creates the VCD file to be used for waveform
viewing
    $dumpvars(0, tb_top_module); // Dump all variables of the testbench
end

endmodule

```

## Results


```

[2024-10-24 21:01:51 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
VCD info: dumpfile waveform.vcd opened for output.

```

```
Time = 0 | A = 0, B = 0, C = 0 -> X = 0, Y = 0
Time = 10000 | A = 0, B = 0, C = 1 -> X = 0, Y = 1
Time = 20000 | A = 0, B = 1, C = 0 -> X = 0, Y = 1
Time = 30000 | A = 0, B = 1, C = 1 -> X = 0, Y = 1
Time = 40000 | A = 1, B = 0, C = 0 -> X = 0, Y = 0
Time = 50000 | A = 1, B = 0, C = 1 -> X = 1, Y = 1
Time = 60000 | A = 1, B = 1, C = 0 -> X = 1, Y = 1
Time = 70000 | A = 1, B = 1, C = 1 -> X = 1, Y = 1
testbench.sv:52: $finish called at 80000 (1ps)
```

Done

 

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.